

## **Graphics Chip Supply Delivers 1.65V at 26A**

Game boxes are using more powerful processors to provide more realistic and complex graphics and games. As the processor power increases, so does the current required to power the parts. The MAX1954 in the application pictured below delivers 1.65V @ 26A from a 5V input.

Game boxes are using more powerful processors to provide more realistic and complex graphics and games. As the processor power increases, so does the current required to power the parts. The MAX1954 in the application pictured below delivers 1.65V @ 26A from a 5V input.

The MAX1954 is a 300kHz current-mode step-down controller. The MOSFET drivers are strong enough to handle 100nC gate charge. Given the nominal input and output voltages, the duty cycle is 33% and the on-resistance of the high- and low-side FETs are skewed accordingly. Two IRF7811W with  $12m\Omega$  on-resistance each are used for the high-side and two IRF7822 with  $6.5m\Omega$  on-resistance each are used for the low-side. Two IRF7811W in parallel have better switching characteristics than one IRF7822.

Seven 22uF/6V X5R ceramic capacitors are used for input bypassing to handle the 12.5Arms input ripple current. At 5V input, ceramic capacitors are more cost effective and smaller than electrolytics. In addition, the MAX1954 senses current by looking at the voltage across the high-side FET on-resistance and ceramic bypass capacitors provide a better reference for the current-sense circuitry. A 2.2nF ceramic capacitor is included drain-to-source across each low-side FET to damp the parasitic ringing of the bond-wire inductance with the drain capacitance. This ringing can affect the current-sense circuitry.

The pulse engineering inductor is a custom part designed to handle 70A peak current without saturating. The MAX1954 uses a "valley" current limit based on the on-resistance of the low-side FET. The current limit is 200mV divided by the low-side FET on-resistance ( $3.3\text{m}\Omega$ ) plus the inductor ramp current (10A) which equals 70A. A 0.5uH/70A inductor is not readily available and a custom design is required to provide short-circuit protection.

The Sanyo output capacitors provide a good balance among ESR, ripple current rating, and cost. The capacitance is large enough for the output ripple to be dominated by the ESR. The application does not require low-profile.


The catch-diode, D2, limits the negative voltage of the LX node when the high-side FET turns off. In conjunction with R4, this controls the voltage on the boost capacitor, C8, at high-line and

maximum output current. Without D2 and R4, the voltage on C8 can BST to LX absolute maximum voltage of 6V.

The MAX1954 delivers 1.65V @ 26A from a 5V input. The efficiency is 86% at 26A and 90% at 10A. The output ripple is 25mVpp.

Table 1.

Vin	lin	Vout	lout	Efficiency
5.0081	0.086	1.6663	0	
4.4905	11.13	1.6547	26	0.861
5.0125	9.95	1.6530	26	0.862
5.509	9.04	1.6513	26	0.862
		25mVpp		

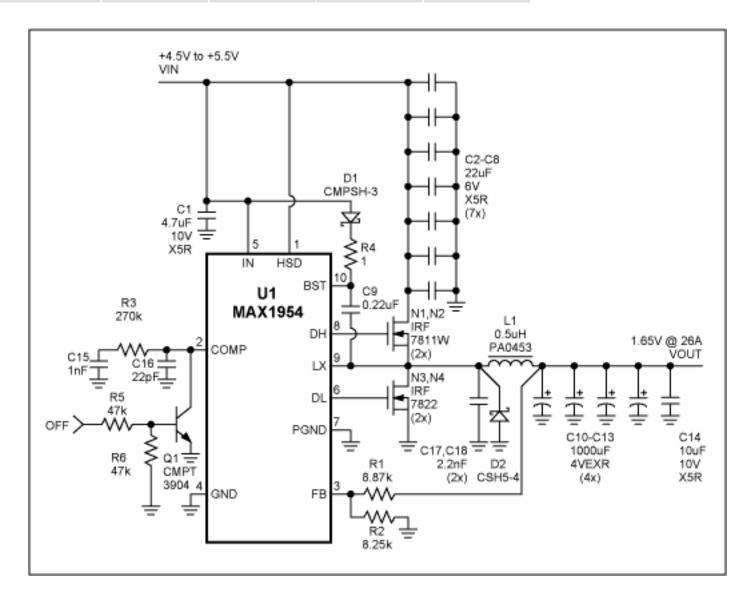

The MAX1954 Bill of Materials: 4.5V to 5.5V Input, 1.65V @ 26A Output

Figure 1.

Designation	Qty	Description	
C1	1	4.7uF 10V X5R ceramic capacitor (1206) Taiyo Yuden LMK316BJ475ML	
C2-C8	7	22uF 6V X5R ceramic capacitor (1210) Taiyo Yuden JMK325BJ226MN	
C9	1	0.22uF ceramic capacitor (0603)	
C10-C13	4	1000uF 4V aluminum electrolytic capacitor Sanyo 4MV1000EXR	
C14	1	10uF 10V X5R ceramic capacitor (1210) Taiyo Yuden LMK325BJ106MN	
C15	1	1nF ceramic capacitor (0603) Kemet C0603C102K8RAC	
C16	1	100pF ceramic capacitor (0603) Kemet C0603C101K5GAC	
C17, C18	2	2.2nF ceramic capacitor (0603) Kemet C0603C222K8RAC	
D1	1	100mA 30V Schottky diode Central Semi CMPSH-3	
L1	1	0.5uH 30A Inductor Pulse Engineering PA0453	
N1, N2	2	12m Ohm 30V N-ch MOSFET (SO-8) International Rectifier IRF7811W	
N3, N4	2	6.5m Ohm 30V N-ch MOSFET (SO-8) International Rectifier IRF7822 or Siliconix Si4842DY	
Q1	1	NPN Transistor (SOT-23) Central Semi CMPT3904	
R1	1	8.87k Ohm 1% resistor (0603)	
R2	1	8.25k Ohm 1% resistor (0603)	
R3	1	270k Ohm 5% resistor (0603)	
R4	1	1 Ohm 5% resistor (0603)	
R5, R6	2	47k Ohm 5% resistor (0603)	
U1	1	MAX1954EUB (10-uMAX)	

## **More Information**

MAX1954: QuickView -- Full (PDF) Data Sheet